

# Main Outlines


- ☐ Review of self inductance
- ☐ Concept of mutual inductance
- ☐ Mutual inductance in terms of self inductance
- ☐ Polarity of the mutually induced voltages (Dot Convention)
- ☐ Procedure for determining dot marking
- ☐ Use of dot markings in circuit analysis



# Self Inductance (Summary)

$$W = \frac{(N i)}{\mathfrak{R}} = (N i)$$

$$\} = N W = L i$$

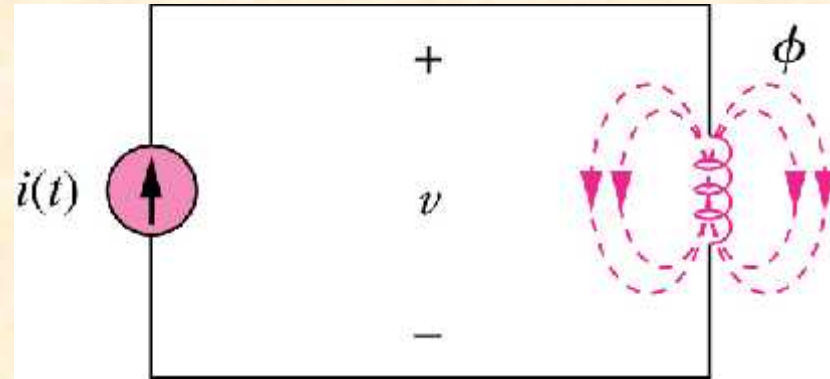

**Magnetic flux produced by a single coil**

$$v = \frac{d\}}{dt} \left\{ \begin{array}{l} v = N \frac{dW}{dt} \\ v = L \frac{di}{dt} \end{array} \right.$$


$$L = \frac{N^2}{\mathfrak{R}} = N^2$$



# Mutual Inductance (Summary)


$$v_1 = N_1 \frac{d\psi_1}{dt}$$

$$v_1 = L_1 \frac{di_1}{dt}$$

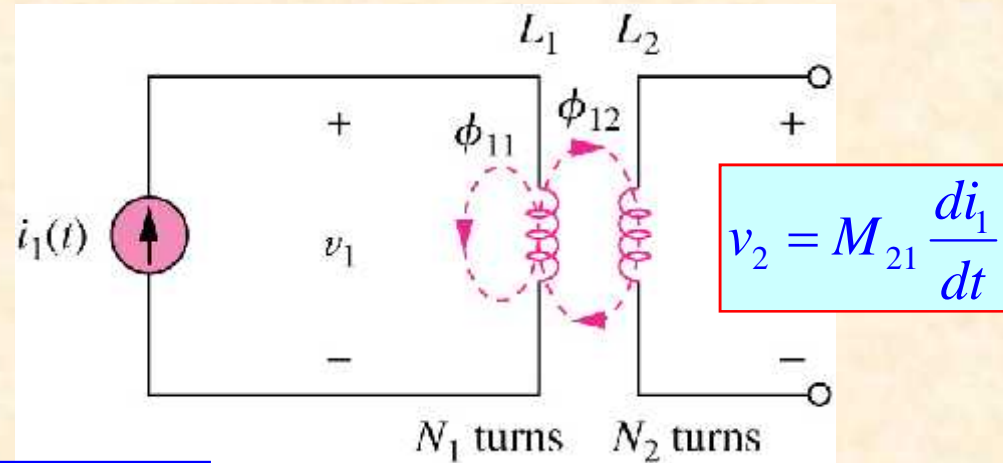

$$M_{21} = M_{12} = M$$

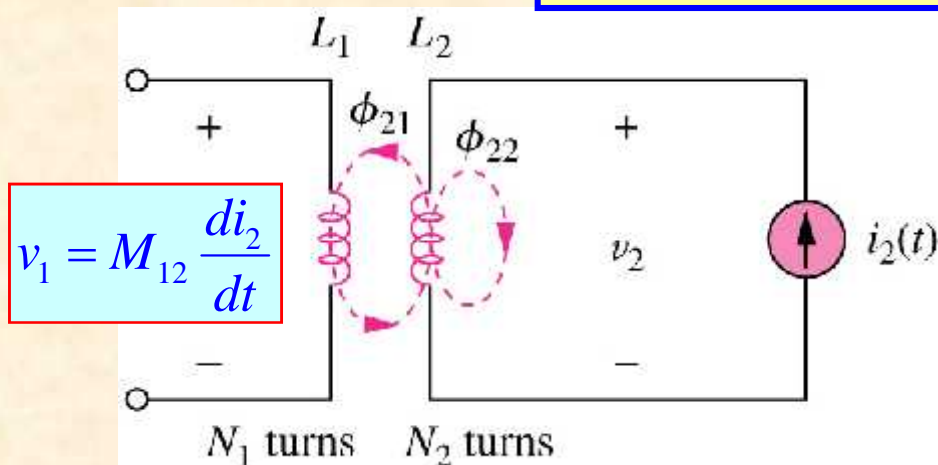**Mutual inductance  $M_{21}$  of coil 2 with respect to coil 1**



$$v_2 = N_2 \frac{d\psi_2}{dt}$$

$$v_2 = L_2 \frac{di_2}{dt}$$

**Mutual inductance of  $M_{12}$  of coil 1 with respect to coil 2**



# Mutual inductance in terms of self inductances (Summary)

$$L_1 = N_1^2 \quad 1$$

$$1 = 11 + 21$$

$$L_2 = N_2^2 \quad 2$$

$$2 = 22 + 12$$

$$M = N_1 N_2 \quad 21$$

$$L_1 L_2 = M^2 \left( 1 + \frac{11}{12} \right) \left( 1 + \frac{22}{12} \right)$$

$$\frac{1}{k^2} = \left( 1 + \frac{11}{12} \right) \left( 1 + \frac{22}{12} \right)$$

$$M = k \sqrt{L_1 L_2}$$

“k” is called the coupling coefficient



# Coupling Coefficient (Summary)

➤ The coupling coefficient “**k**” is a measure of the percentage of flux from one coil that links another coil

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

□ Range of **k** : 0 ≤ k ≤ 1

- If **k > 0.5** , the coils are said to be **tightly coupled**
- If **k < 0.5**, the coils are said to be **loosely coupled**
- **k = 0** means the two coils are **not coupled**
- **k = 1** means the two coils are **perfectly coupled**

**k** can be expressed in terms of flux as

$$k = \frac{W_{12}}{W_{11} + W_{12}}$$

or  $k = \frac{W_{21}}{W_{21} + W_{22}}$


**k = 1** means perfect coupling.

$$\Rightarrow W_{11} = W_{22} = 0$$





# Magnetically Coupled Circuits

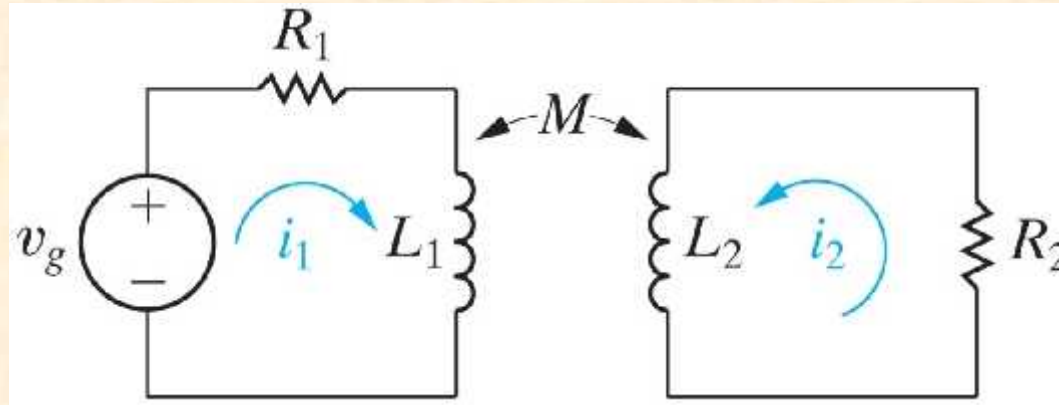

□ There will be **two voltages** across each coil;

✓ “self-induced” voltage,  **$L(di/dt)$** , and

✓ “mutually induced” voltage,  **$M(di/dt)$**

➤ The polarity of the self-induced voltage is the same as the **resistive voltage drop**

➤ The polarity of the mutually induced voltage can be determined according to **Lenz's Law**



# Magnetically Coupled Circuits

$$\lambda_1(t) = L_1 i_1(t) + M_{12} i_2(t)$$


$$\lambda_2(t) = M_{21} i_1(t) + L_2 i_2(t)$$

$$v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$v_2 = \frac{d\lambda_2}{dt} = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

**Mutual induced voltage**

**Self induced voltage**

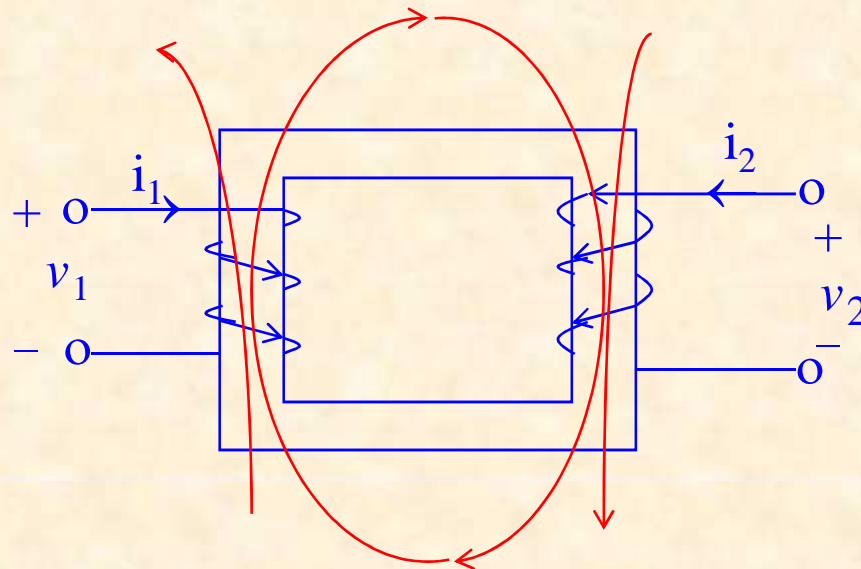

# Magnetically Coupled Circuits

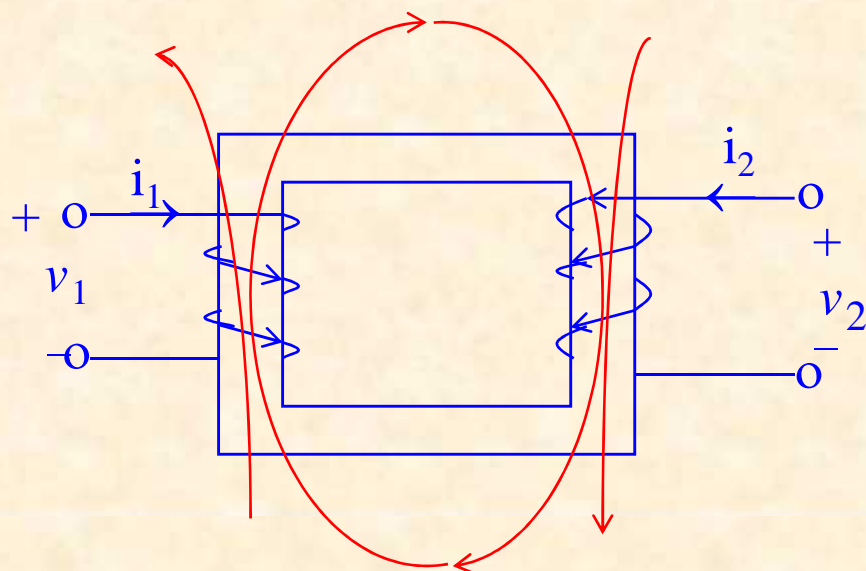


$$\lambda_1(t) = L_1 i_1(t) + M i_2(t)$$

$$\lambda_2(t) = M i_1(t) + L_2 i_2(t)$$

$$v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
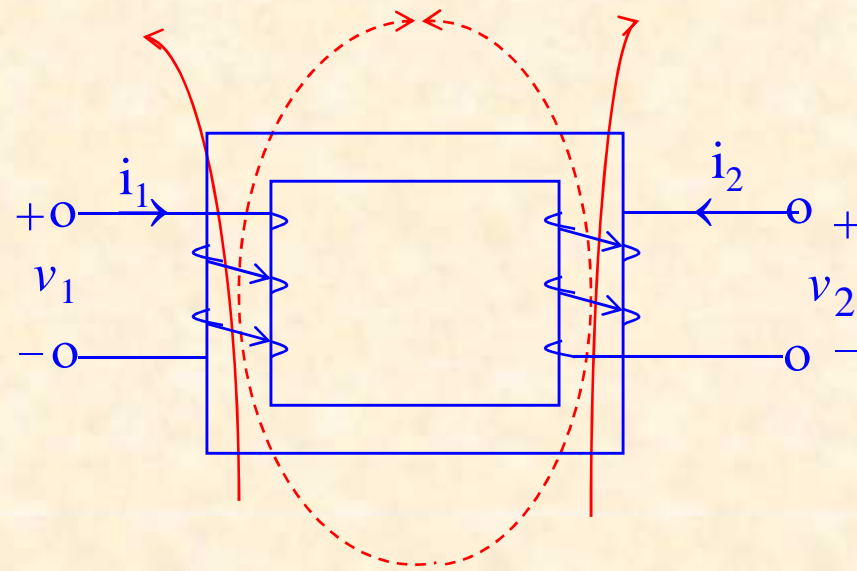
$$v_2 = \frac{d\lambda_2}{dt} = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



$$\lambda_1(t) = L_1 i_1(t) - M i_2(t)$$

$$\lambda_2(t) = -M i_1(t) + L_2 i_2(t)$$


$$v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = \frac{d\lambda_2}{dt} = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$





# Magnetically Coupled Circuits

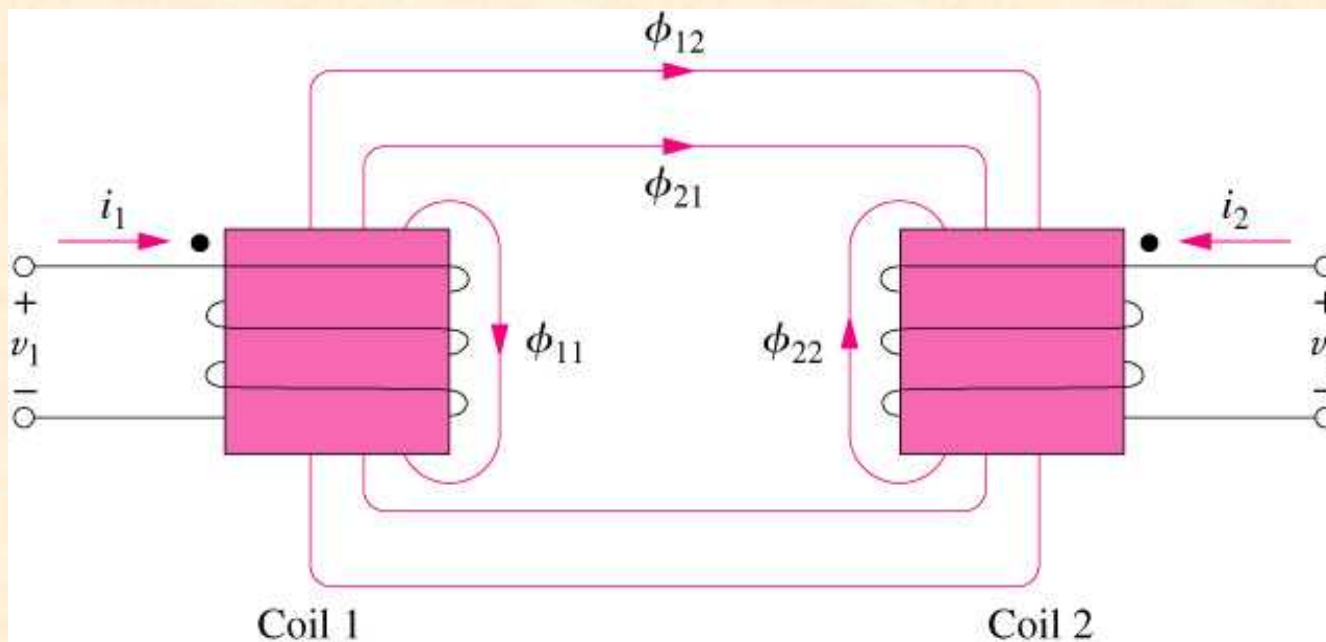

$i_1$  induces  $w_{11}$  and  $w_{12}$ ,

$i_2$  induces  $w_{21}$  and  $w_{22}$ .

$$W_1 = (w_{11} + w_{12}) + w_{21}$$

$$W_2 = w_{12} + (w_{21} + w_{22})$$


$$v_1 = N_1 \frac{dW_1}{dt} = N_1 \frac{d(w_{11} + w_{12})}{dt} + N_1 \frac{dw_{21}}{dt} = L_1 \frac{di_1}{dt} + M_{12} \frac{di_2}{dt}$$

$$v_2 = N_2 \frac{dW_2}{dt} = N_2 \frac{d(w_{21} + w_{22})}{dt} + N_2 \frac{dw_{12}}{dt} = L_2 \frac{di_2}{dt} + M_{21} \frac{di_1}{dt}$$


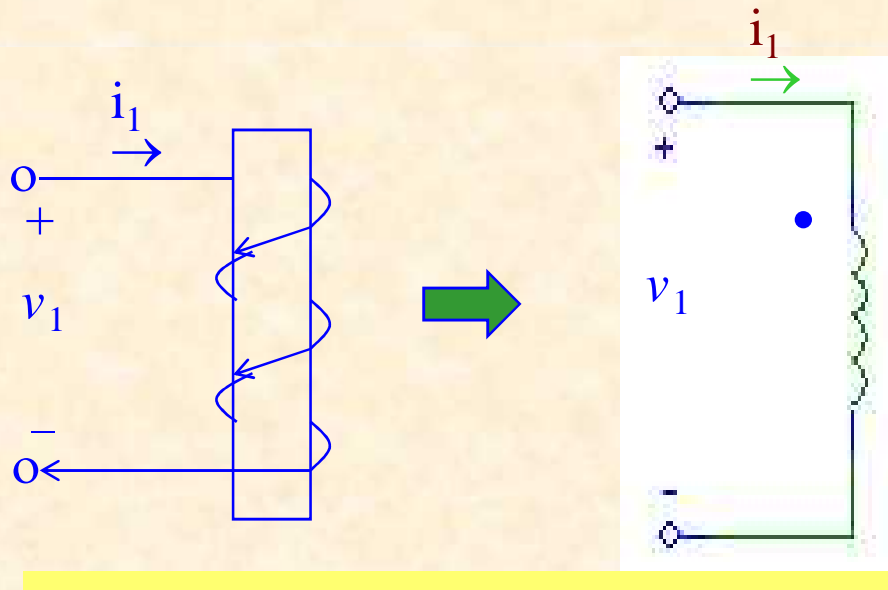
# Dot Convention

- Required to determine polarity of “mutual” induced voltage
- A **dot** is placed in the circuit at one end of each of the two magnetically coupled coils to indicate the direction of the magnetic flux if current enters that dotted terminal of the coil




**Dot indicate the direction in which the coils are wound**

**Lumped Coil Representation**



# Dot Convention

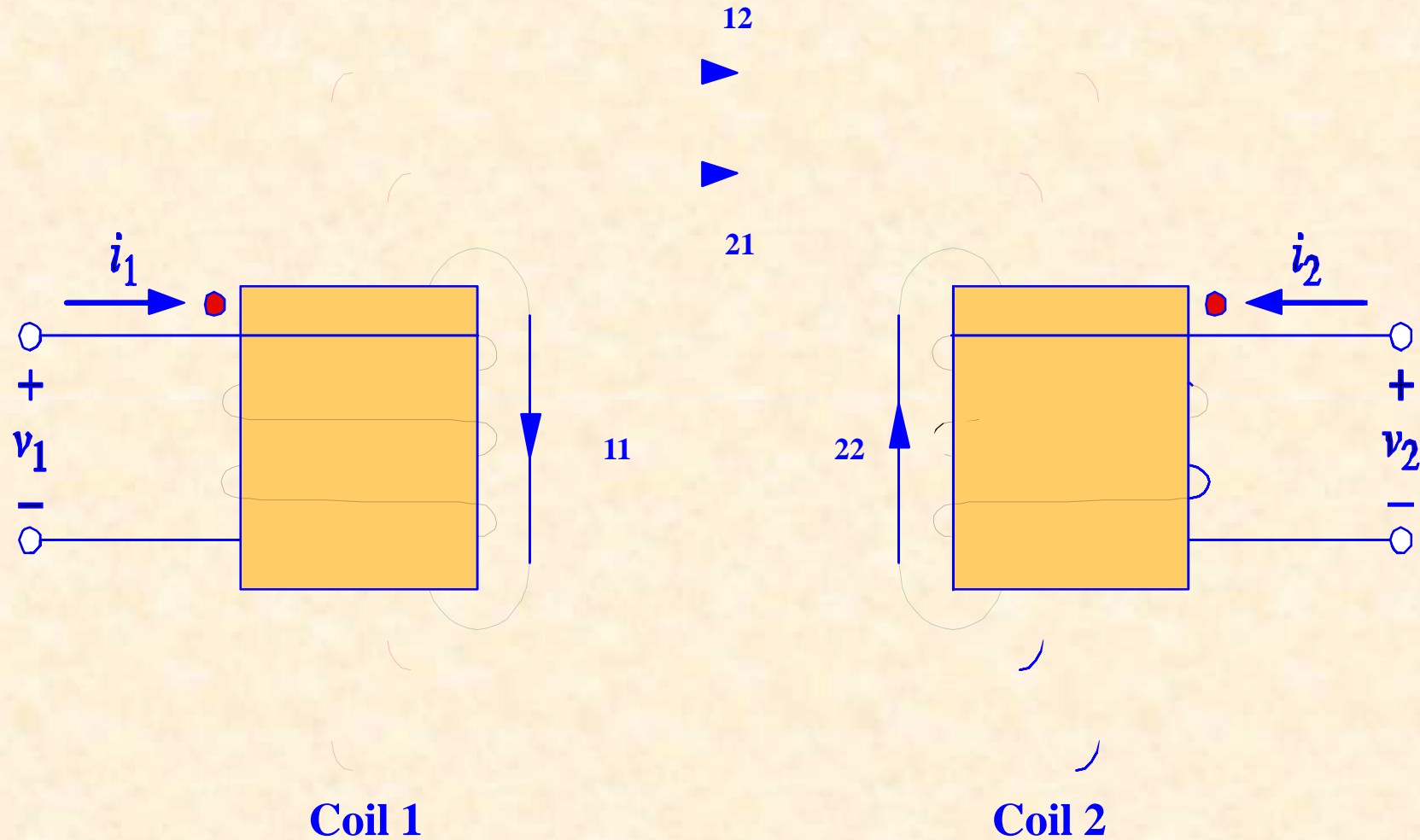

# Dot Convention

□ Dot convention is stated as follows:

- ✓ if a current **ENTERS** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **POSITIVE** at the dotted terminal of the second coil



□ Conversely, Dot convention may also be stated as follow:

- ✓ if a current **LEAVES** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **NEGATIVE** at the dotted terminal of the second coil


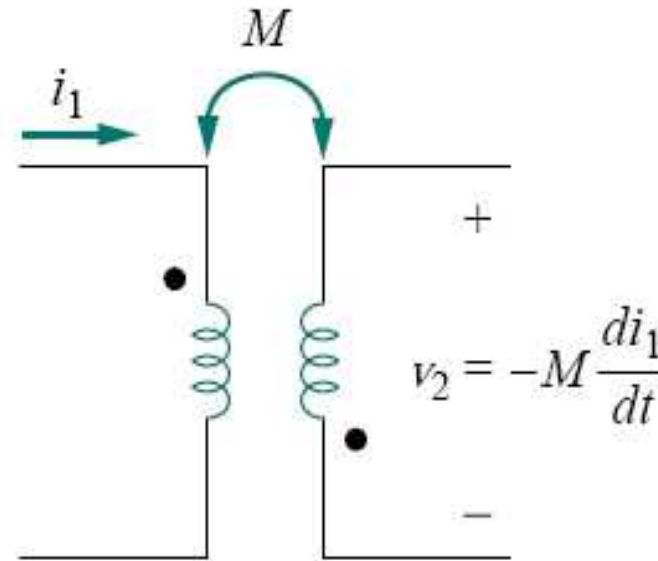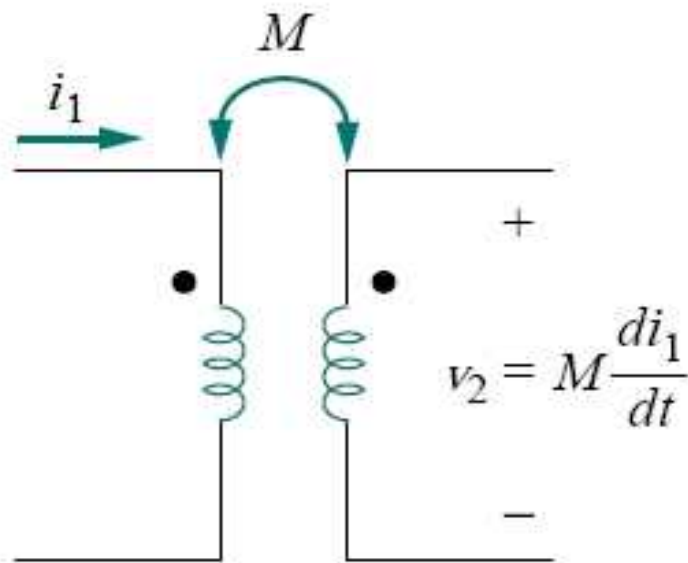
# Dot Convention


If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.








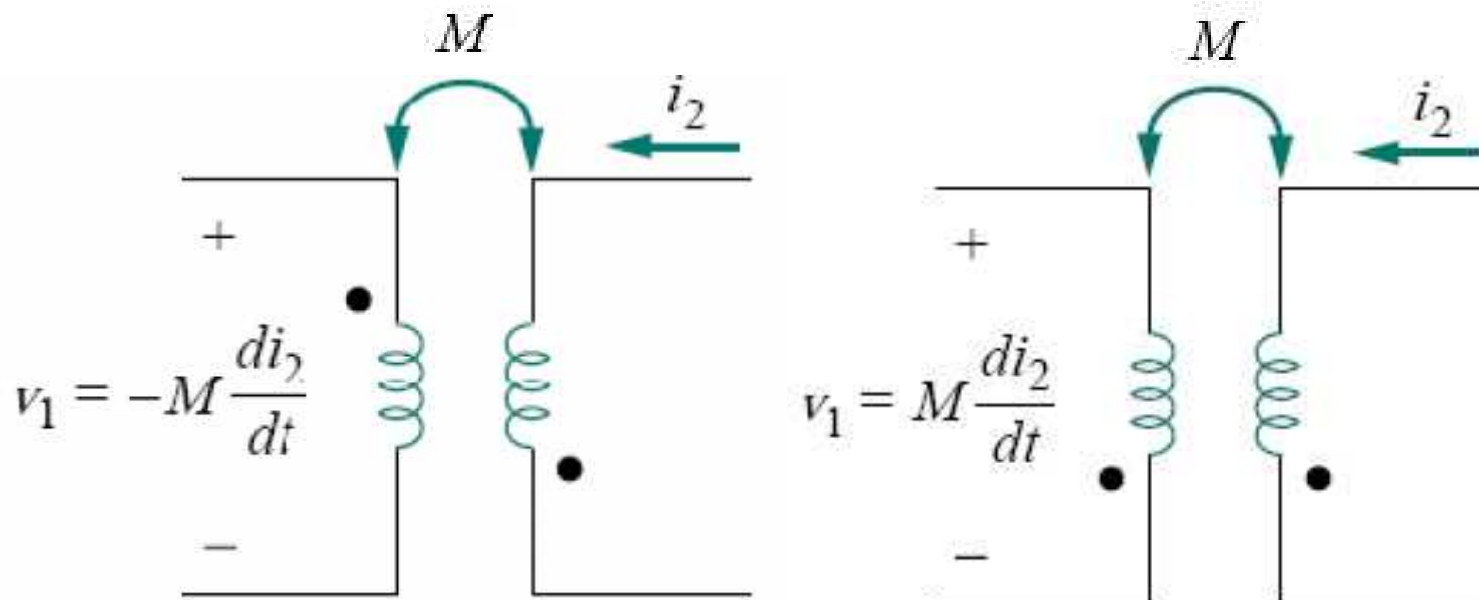
# Dot Convention

If a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.



# Dot Convention

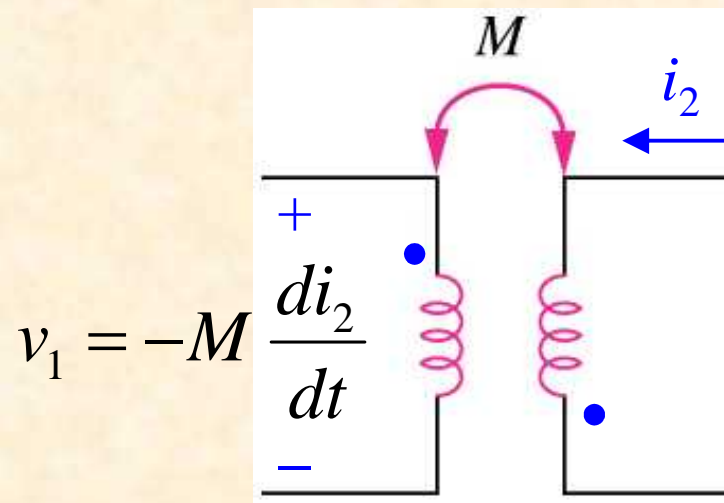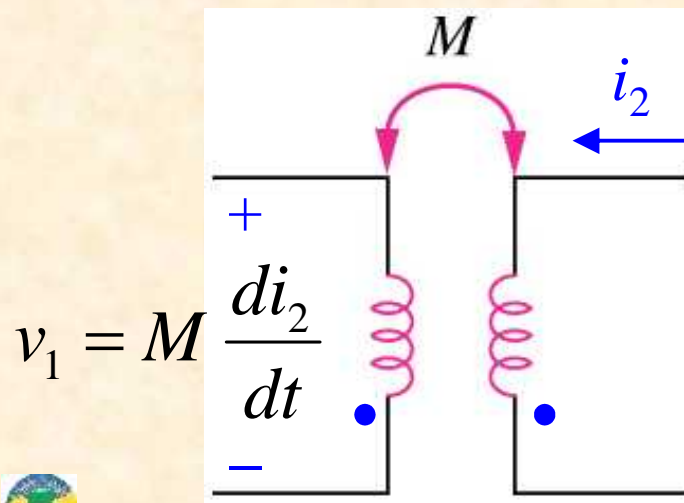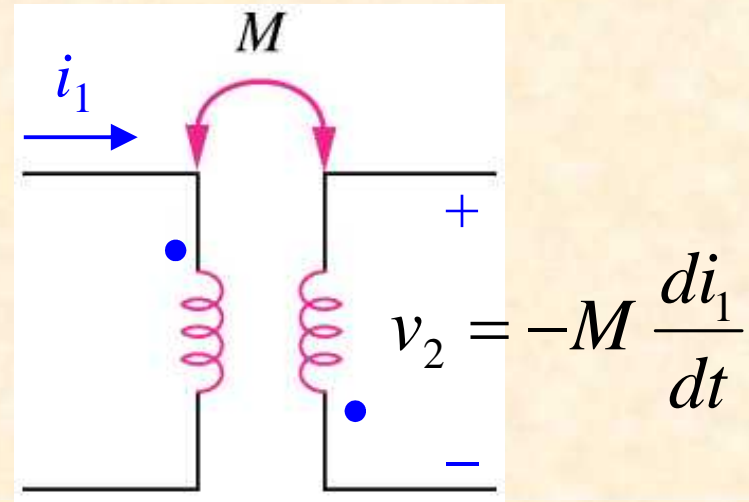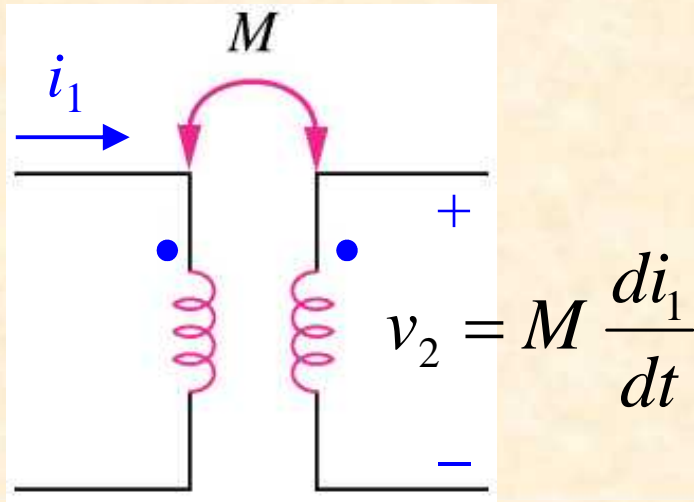


# The Rule for using the Dot Convention

- ❑ The following dot rule may be used:
- ✓ When the assumed currents **both entered or both leaves** a pair of coupled coils by the dotted terminals, the signs on the **L – terms** will be **the same** as the signs on the **M – terms**
- ✓ If one current **enters** by a dotted terminals while the other **leaves** by a dotted terminal, the sign on the **M – terms** will be **opposite** to the signs on the **L – terms**.





# The Rule for Using the Dot Convention

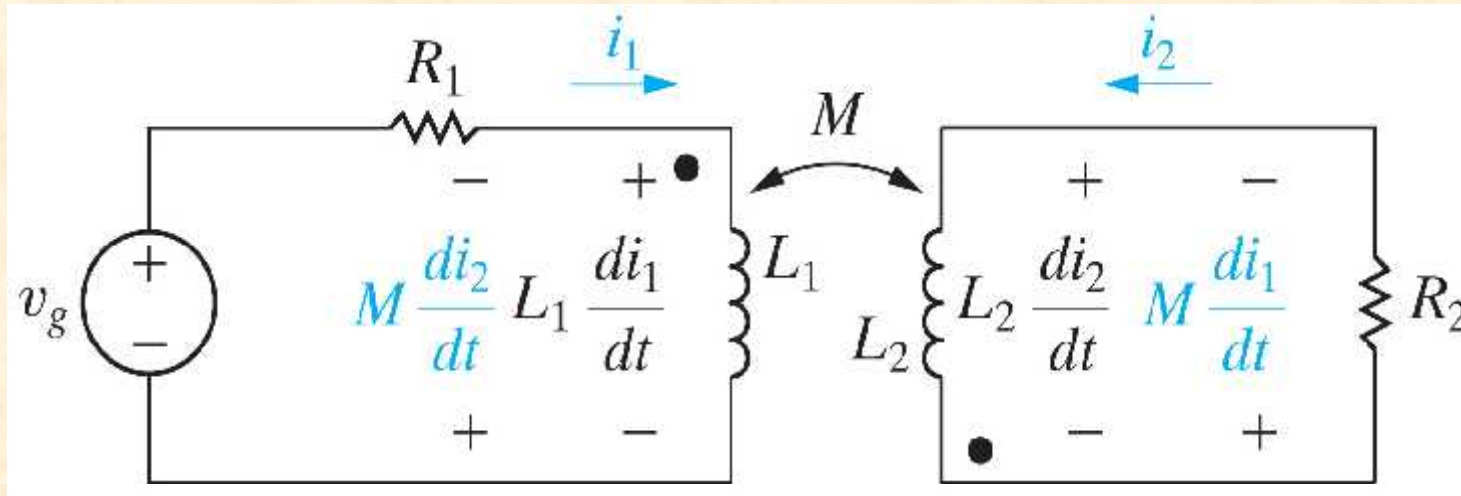

- ✓ The voltage induced in coil 1 by the current in coil 2 is **negative** at the dotted terminal of coil 1
- ✓ The voltage induced in coil 2 by the current in coil 1 is **positive** at the dotted terminal of coil 2




# The Rule for Using the Dot Convention

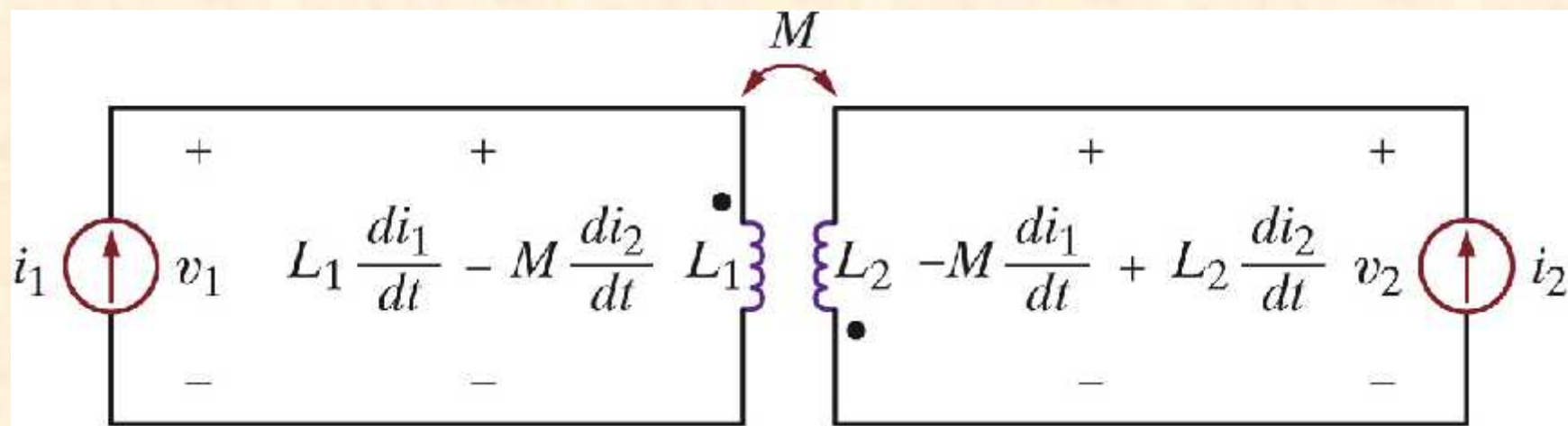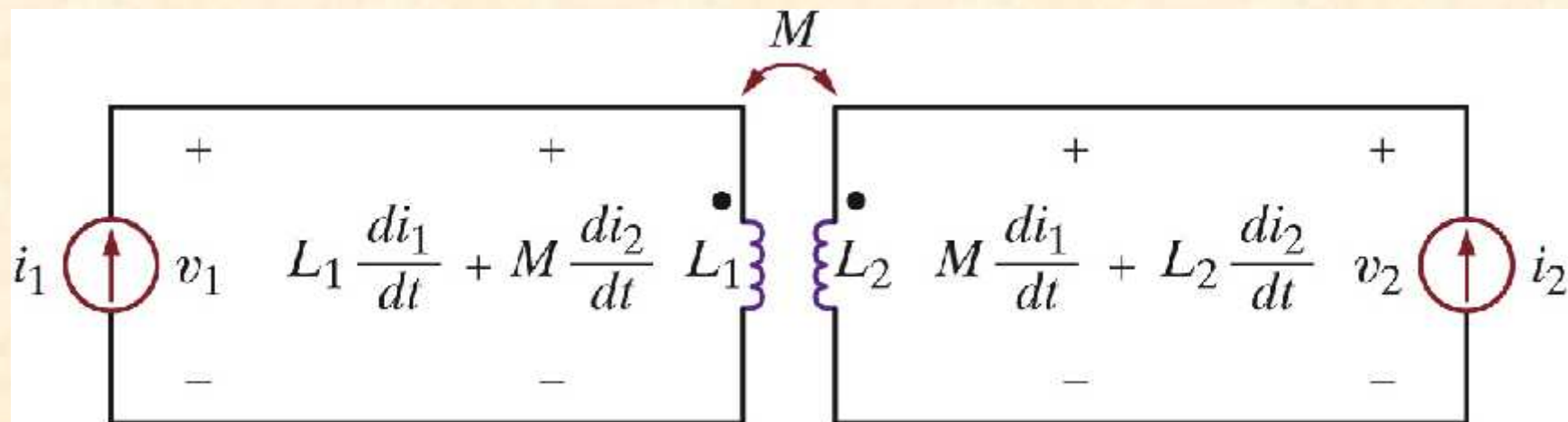



# Dot Convention for Coils in Series

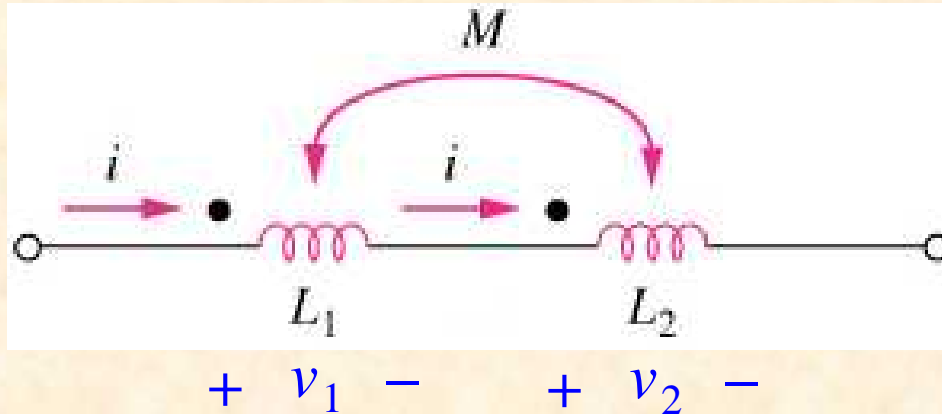

$$L = L_1 + L_2 + 2M$$

(series - aiding connection)

$$v_1 = L_1 \frac{di}{dt} + M_{12} \frac{di}{dt}$$

$$v_2 = L_2 \frac{di}{dt} + M_{21} \frac{di}{dt}$$

$$v = v_1 + v_2$$

$$= L_1 \frac{di}{dt} + M_{12} \frac{di}{dt} + L_2 \frac{di}{dt} + M_{21} \frac{di}{dt}$$

$$= (L_1 + L_2 + M_{12} + M_{21}) \frac{di}{dt}$$


But  $M_{12} = M_{21} = M$ ,

$$\Rightarrow v = (L_1 + L_2 + 2M) \frac{di}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2 + 2M$$



# Dot Convention for Coils in Series

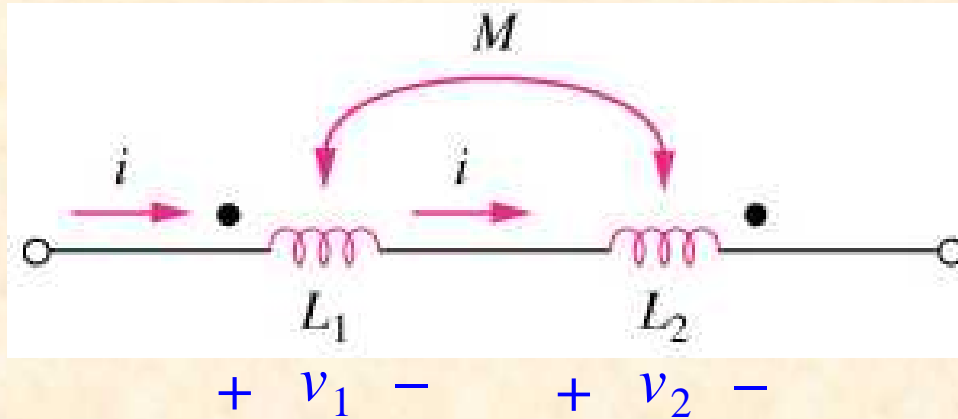

$$L = L_1 + L_2 - 2M$$

(series - opposition connection)

$$v_1 = L_1 \frac{di}{dt} - M_{12} \frac{di}{dt}$$

$$v_2 = L_2 \frac{di}{dt} - M_{21} \frac{di}{dt}$$

$$v = v_1 + v_2$$

$$= L_1 \frac{di}{dt} - M_{12} \frac{di}{dt} + L_2 \frac{di}{dt} - M_{21} \frac{di}{dt}$$

$$= (L_1 + L_2 - M_{12} - M_{21}) \frac{di}{dt}$$


But  $M_{12} = M_{21} = M$ ,

$$\Rightarrow v = (L_1 + L_2 - 2M) \frac{di}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2 - 2M$$




# Circuit Model for Coupled Inductors

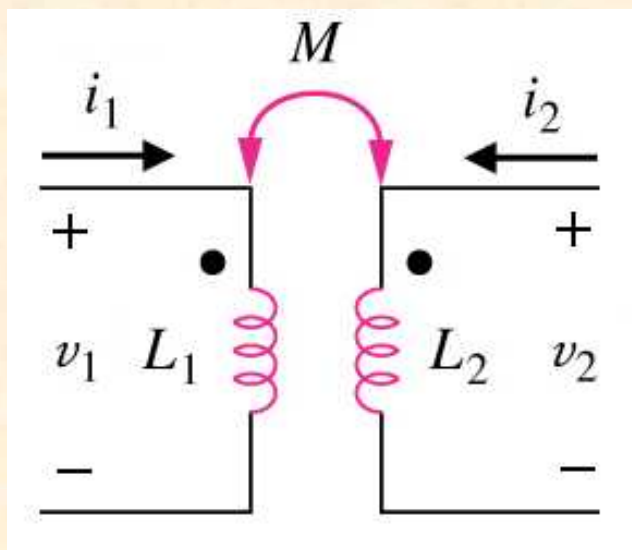

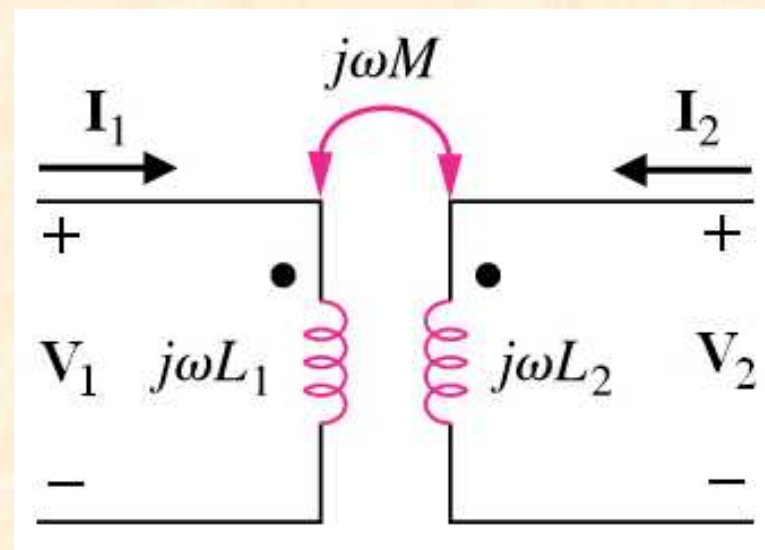**Time-domain circuit**

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$




**Frequency-domain circuit**

$$\mathbf{V}_1 = j\check{S}L_1\mathbf{I}_1 + j\check{S}M\mathbf{I}_2$$

$$\mathbf{V}_2 = j\check{S}M\mathbf{I}_1 + j\check{S}L_2\mathbf{I}_2$$



# Mesh Equations using Dot Convention

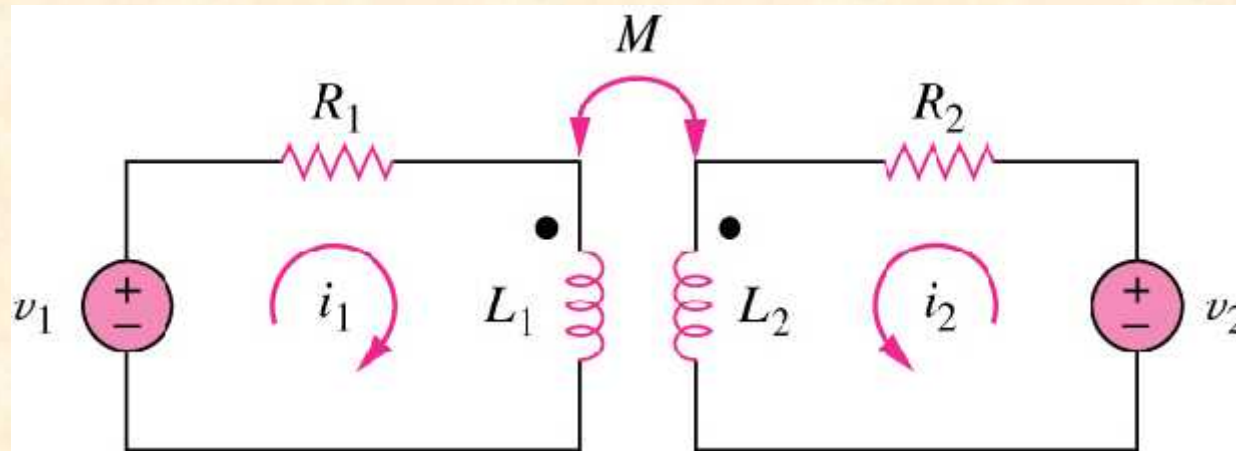

Applying KVL to mesh 1 gives

$$v_1 = i_1 R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

Applying KVL to mesh 2 gives

$$v_2 = i_2 R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

In phasor (frequency ) domain

$$\mathbf{V}_1 = (R_1 + j\check{S}L_1)\mathbf{I}_1 + j\check{S}M\mathbf{I}_2$$

$$\mathbf{V}_2 = j\check{S}M\mathbf{I}_1 + (R_2 + j\check{S}L_2)\mathbf{I}_2$$

